

[22-HKPD1SN-23A]

DCA/PGDCA/MScIT 1st Semester (New) Exam. 2022 (W)

(*Digital Techniques*)

[PGCA/SCIT S1-02]

Full Marks : 70/80

Time : 3 hours

The figures in the right-hand margin indicate marks.

[Learners admitted in and after 2020 need to answer only Q.No. 1 to Q.No. 4 (total 70 marks)]

1. Answer any *five* of the following questions : 2 × 5 = 10

- (a) Differentiate between combinational and sequential circuit specifying the block diagram of each case.
- (b) State the truth table for full adder.
- (c) Mention the different approaches of representing a fixed point binary number.
- (d) Add two BCD numbers 00100011 and 00010001.
- (e) What are the formats to represent a floating point number in IEEE standard ?
- (f) Write the purpose of cache memory.

2. Answer any *four* of the following questions : 3 × 4 = 12

- (a) What is shift registers ? Mention different categories of shift registers.

(Turn Over)

(2)

- (b) Express the Boolean function $xy + xz' + y'$ in a sum of minterms.
- (c) Write the purpose of using 4-bit binary parallel adder. Draw a 4-bit binary parallel adder.
- (d) Give the differences between asynchronous and synchronous counter. What do you mean by modulus of a counter?
- (e) Mention the steps to convert a binary number into Gray Code.

3. Answer any *four* of the following questions : 6 × 4 = 24

- (a) Define flip-flop. Discuss JK flip-flop with a block diagram.
- (b) Convert a binary number $(1011.011)_2$ into (i) Octal, (ii) Decimal and (iii) Hexadecimal format.
- (c) Discuss about different categories of RAM.
- (d) What is de-multiplexer? With the suitable diagram explain 1-to-16 de-multiplexer.
- (e) Simplify the Boolean function with K-map :

$$F = A'B'C' + B'CD' + A'BCD' + A'BC'$$

4. Answer any *three* of the following questions : 8 × 3 = 24

- (a) Convert a decimal number $(860.12)_{10}$ to a 32-bit single precision floating point binary no.
- (b) What is logic family? Discuss briefly about Resistor Transistor Logic.
- (c) Why are NAND and NOR gates called universal gates? Explain the operation of 2-input XOR gate and realise it using NAND/NOR gates.
- (d) Add 27 and -35 in binary using 7 bit register in 2'S complement form.

(Continued)

(3)

(Q. No. 5 is only for learners admitted before 2020)

5. Answer any *one* of the following questions :

10 × 1 = 10

- (a) Design a 3-to-8 decoder with its truth table.
- (b) Discuss how a semiconductor RAM is arranged. Draw the block diagram of a RAM chip.